

CSC 258 midterm solutions

27 February 2002, 11:00

1. a) What function does the following logic gate diagram compute?
[not shown here; see the test paper]

Answer: $x(xy \oplus xyz)$

- b) Simplify this formula (using any appropriate technique).

Answer:

$$\begin{aligned} & x(xy \oplus xyz) \\ &= x((xy)xyz + xy(\overline{xyz})) \\ &= x((\bar{x} + \bar{y})xyz + xy(\bar{x} + \bar{y} + \bar{z})) \\ &= x\bar{x}xyz + x\bar{y}xyz + xxy\bar{x} + xxy\bar{y} + xxy\bar{z} \\ &\quad \text{(you may prefer to expand to that in two or three steps, but it does all multiply through)} \\ &= 0 + 0 + 0 + 0 + xy\bar{z} \\ &= xy\bar{z} \end{aligned}$$

- c) Draw a logic gate diagram for your simplified formula.


[answer not shown here]

2. Here is a three-bit ripple counter.

[standard ripple counter picture went here, similar to the answer below]


Draw a three-bit counter with *two* inputs: an “add one” input such as above, and a “complement” input which toggles all three bits (e.g. 010 will become 101).

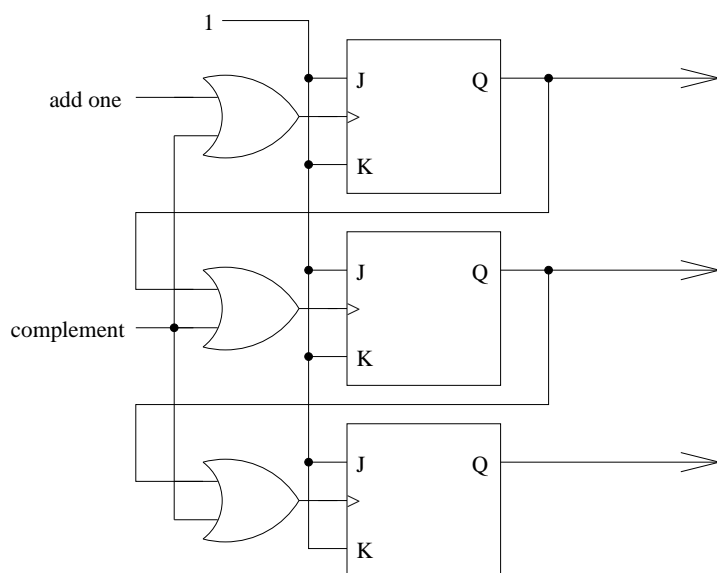You can assume that these two inputs will never be 1 at the same time.



(over)

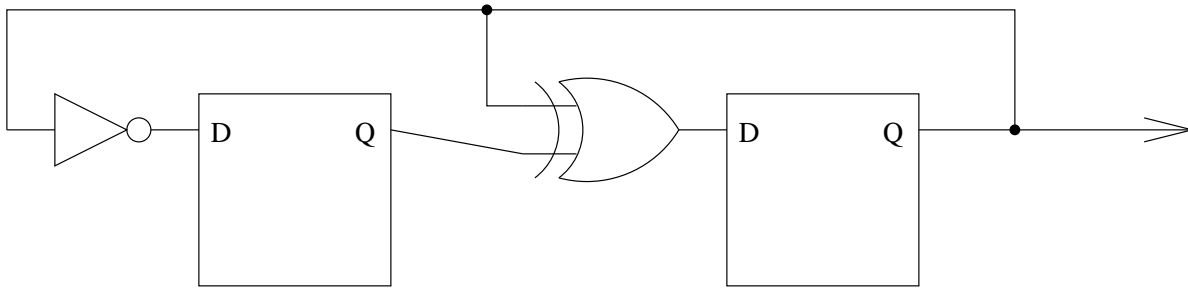3. What is the output sequence of the following “counter”, after it gets established in its cycle?



Answer: either 0,0,1,0,0,1,0,0,1,... or staying at 1, depending upon initial state.

4. a) Here are some four-bit addition problems, some of which will overflow. Complete the addition operation and state the base-ten value of the operands and the result.

Question and answers combined:

0001	0111	0100	0101	1000	0001
+0010	+0010	+0011	+0011	+1000	+1011
-----	-----	-----	-----	-----	-----
0011	1001	0111	1000	0000	1100
1+2=3	7+2=-7	4+3=7	5+3=-8	-8+-8=0	1+-5=-4

b) Show that overflow is *not* the same as carry out (from the entire addition, i.e. c_n) by using one of the examples above.

Answer: Either $7+2=-7$ or $5+3=-8$ would do; in both of these examples, overflow = 1 and carry-out = 0.